

Course outline

How does an NPTEL online course work?

Week 0

Quiz: Assignment 0

Week 1

Week 2

Week 3

Week 4

Week 5

Week 6

Week 7

Week 8

Assignments Solution

Download Videos

Text Transcripts

Live Interactive session

Books

Assignment 0

The due date for submitting this assignment has passed.

Due on 2021-07-26, 23:59 IST.

As per our records you have not submitted this assignment.

1) What will be the 12-bit binary sign-magnitude representation of decimal number -396? 1 point

- a. 000110001100.
- b. 001110001100
- c. 100110001100
- d. 111110001100

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
c.

2) The smallest binary signed 2's complement 11-bit number is _____ (in decimal). 1 point

HINT: (Specify the number in decimal, e.g. 26, -37, 98 etc.)

No, the answer is incorrect.
Score: 0

Accepted Answers:
(Type: Numeric) -1024

3) The decimal equivalent of the 2's complement number 1001 is _____. 1 point

HINT: (Specify the number in decimal, e.g. 26, -37, 98 etc.)

No, the answer is incorrect.
Score: 0

Accepted Answers:
(Type: Numeric) -7

4) Which of the following statement(s) is/are false regarding 2's complement signed binary addition? 1 point

- a. Adding two n-bit positive numbers causes an overflow if the result is greater than $2^{n-1} - 1$.
- b. Adding two n-bit negative numbers causes an overflow if the result is less than -2^{n-1} .
- c. A carry out of most significant $n - 1^{th}$ bit position during addition of two n-bit numbers indicate overflow.
- d. None of these.


HINT: (If options a, b and c are all true, select option d as the answer.)

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
c.

 5) A lamp (C), two switches (A and B) and a load resistance (R) are connected to a power supply in the following way: 1 point



Considering the lamp-ON/ lamp-OFF as logic 1/0 output and switch-open/switch-close as logic 0/1 input, what logic gate functionality does the network realize?

- a. A 2-input AND gate.
- b. A 2-input NAND gate.
- c. A 2-input OR gate.
- d. A 2-input NOR gate.


- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
b.

6) How many 2-input NOR gate of following type are required to realize a 5-input NOR gate?

1 point

 

- a. 5
- b. 6
- c. 7
- d. 8


- ☐ a.
☐ b.
☐ c.
☐ d.

No, the answer is incorrect.
 Score: 0

Accepted Answers:
 d.

7) What Boolean function is realized by the following NMOS network (Here X' is used to denote complement of X)?

1 point

 

- a. $Y = (A'B + CD')E'$.
- b. $Y = (A' + B)(C + D') + E'$
- c. $Y = (AB' + C'D)E$
- d. None of these.

HINT: (If options a, b and c are all incorrect, select option d as the answer.)

- ☐ a.
☐ b.
☐ c.
☐ d.

No, the answer is incorrect.
 Score: 0

Accepted Answers:
 c.

8) Which of the following set of modules is/are universal ?

1 point

- a. 2-input gate set {AND, OR}
- b. 2-input AND gate and NOT gate
- c. 2-to-1 Multiplexer
- d. 2-input gate set {XOR, AND}

- ☐ a.
☐ b.
☐ c.
☐ d.

No, the answer is incorrect.
 Score: 0

Accepted Answers:
 b.
 c.
 d.

9) How many 2-to-1 multiplexer will be required to realize the following logic function?

1 point

a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- a. 2
- b. 3
- c. 4
- d. 5

- ☐ a.
☐ b.
☐ c.
☐ d.

No, the answer is incorrect.
 Score: 0

Accepted Answers:
 c.

10) Which one is the minimal equivalent expression for the following function:

1 point

$$f = w'x + wxz + wx'yz' + xy$$

- a. $f = w'x + xz + wyz' + xy$
- b. $f = w'x + xy + wx'yz'$
- c. $f = w'x + xz + wyz'$
- d. None of these

HINT: (If options a, b and c are all incorrect, select option d as the answer.)

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
c.

- 11) Which of the following statement(s) is/are true regarding 1's catching problem in SR master-slave flip-flops?

1 point

- a. 1's catching occurs when slave latch is in 0 state and master latch have a static-0 hazard at S-input during the active clock state.
- b. 1's catching occurs when slave latch is in 0 state and master latch have a static-0 hazard at R-input during the active high clock state.
- c. 1's catching occurs when slave latch is in 1 state and master latch have a static-0 hazard at S-input during the active high clock state.
- d. 1's catching occurs when slave latch is in 1 state and master latch have a static-0 hazard at R-input during the active high clock state.

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
a.

- 12) Which flip-flop does not suffer from 0's and 1's catching problem?

1 point

- a. JK
- b. D
- c. T
- d. All of these

HINT: (If options a, b and c are all correct, select option d as the answer.)

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
b.

- 13) Which physical design is not preferable for hardware realization when higher system speed is a requirement?

1 point

- a. Gate Array
- b. FPGA
- c. Standard Cell
- d. Full Custom

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
b.

- 14) Which physical implementation does not require fabrication stage and thus reduces development time and cost?

1 point

- a. Gate Array
- b. FPGA
- c. Standard Cell
- d. Full Custom

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:
b.

- 15) Which of the following statement(s) is/are true regarding simulation and synthesis of logic circuit?

1 point

- a. Simulation is the analysis of a designed circuit model at some higher level of abstraction in a software environment.
- b. Synthesis is the analysis of a designed circuit model at some higher level of abstraction in a software environment.

- c. Synthesis is the process of translating a designed circuit model at some level to the next lower level of abstraction.
- d. Simulation is the process of translating a designed circuit model at some level to the next lower level of abstraction.

- ☐ a.
- ☐ b.
- ☐ c.
- ☐ d.

No, the answer is incorrect.
Score: 0

Accepted Answers:

- a.
- c.

Rate this lesson:

Not at all
useful

Not very
useful

Somewhat
useful

Very useful

Extremely
useful